

Elementos de Lógica Digital II

Aula 4 – Introduction to Moore FSM

Prof. Vanderlei Bonato - vbonato@icmc.usp.br

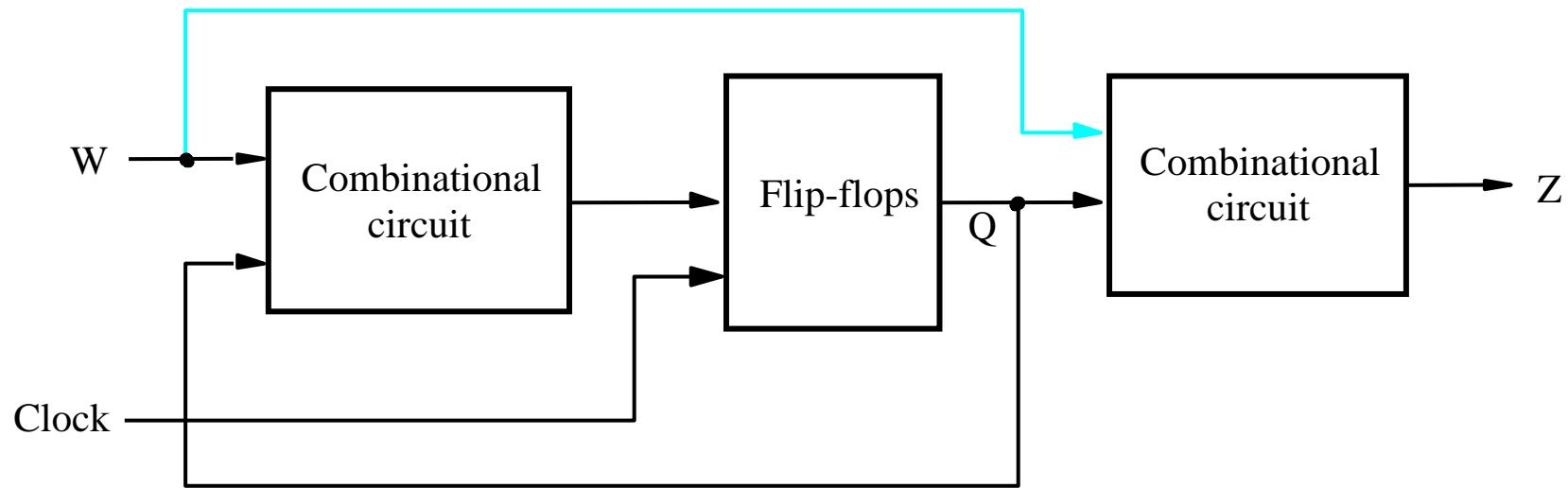


Figure 8.1. The general form of a sequential circuit.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
$w:$	0	1	0	1	1	0	1	1	1	0	1
$z:$	0	0	0	0	0	1	0	0	1	1	0

Figure 8.2. Sequences of input and output signals.

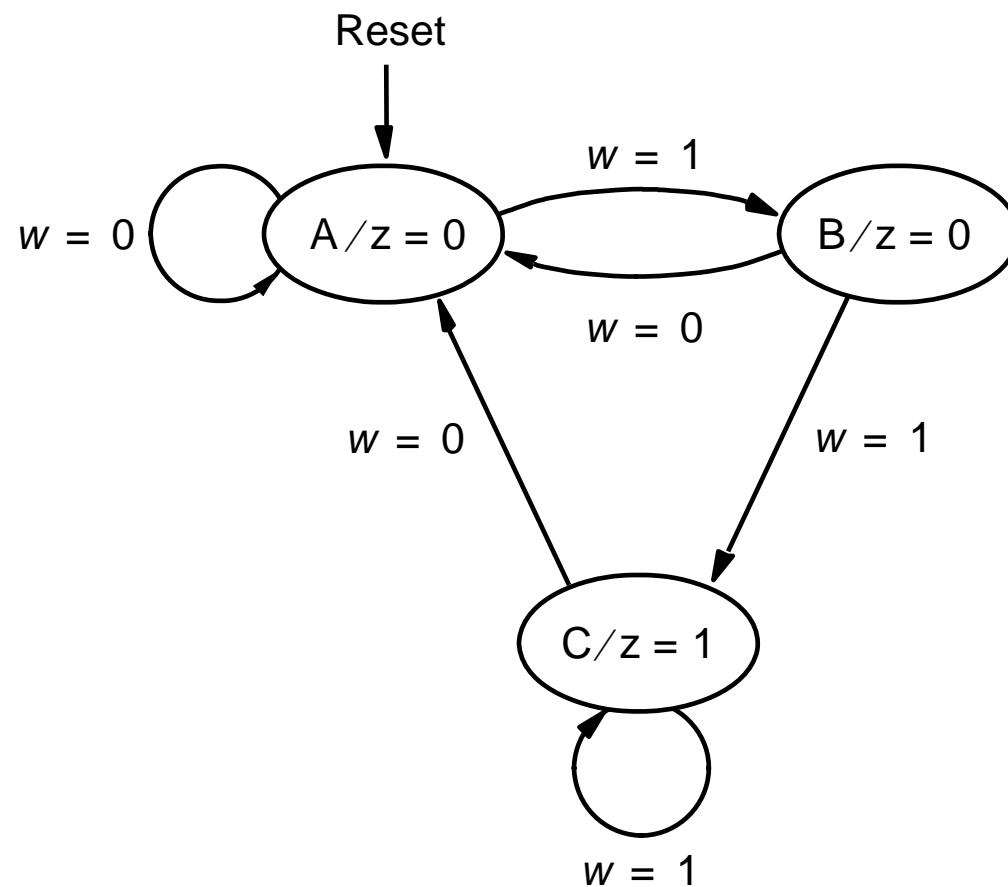


Figure 8.3. State diagram of a simple sequential circuit.

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Figure 8.4. State table for the sequential circuit in Figure 8.3.

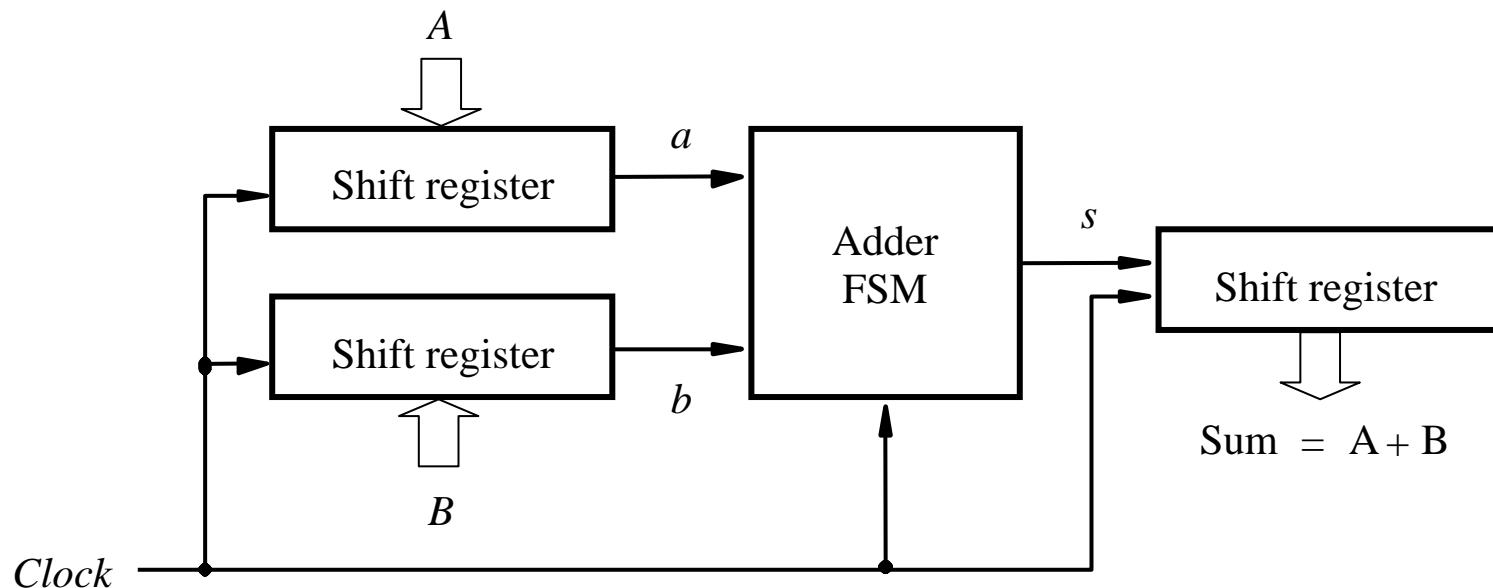


Figure 8.39. Block diagram for the serial adder.

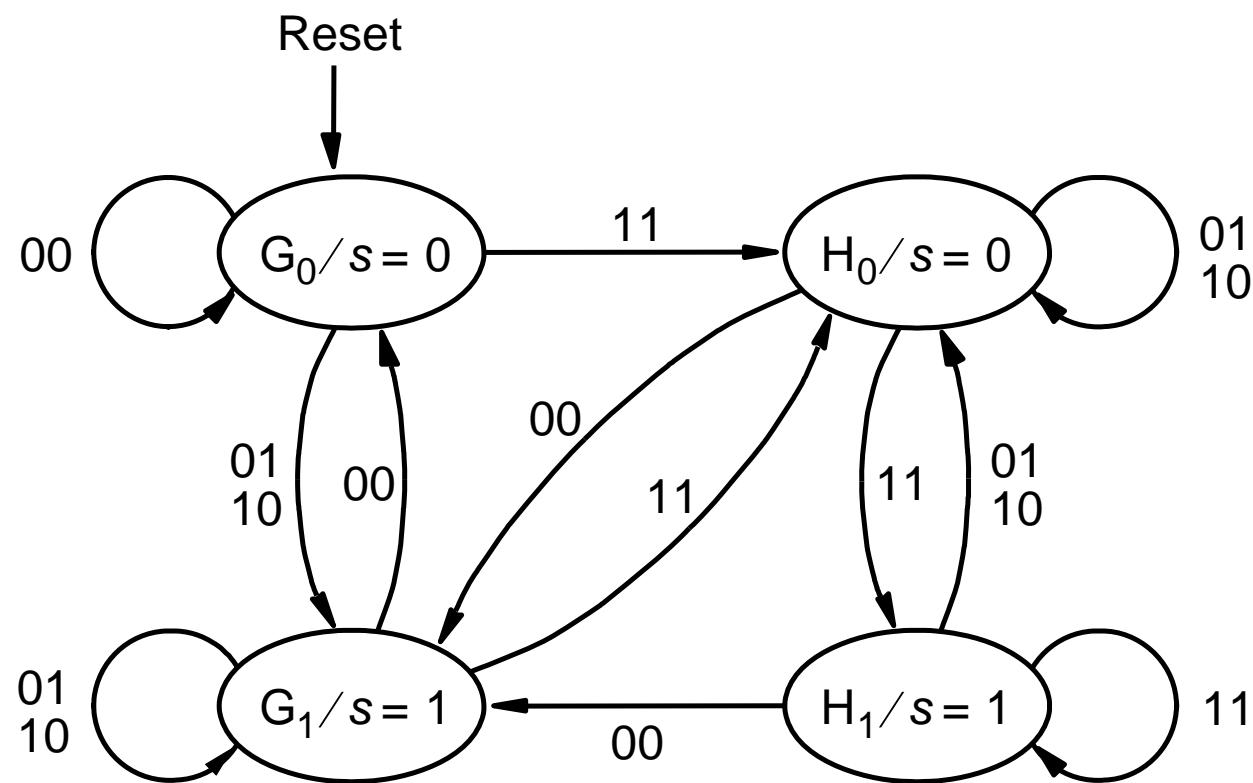


Figure 8.44. State diagram for the Moore-type serial adder FSM.