

SCE 0110 -
Elementos de Lógica Digital I

**Tecnologia de Implementação
(continuação)**

Prof. Vanderlei Bonato

Sumário

- FPGAs e outros dispositivos lógicos programáveis
- Estrutura física de um transistor do tipo MMOS
- Vídeo de uma fábrica virtual de CIs

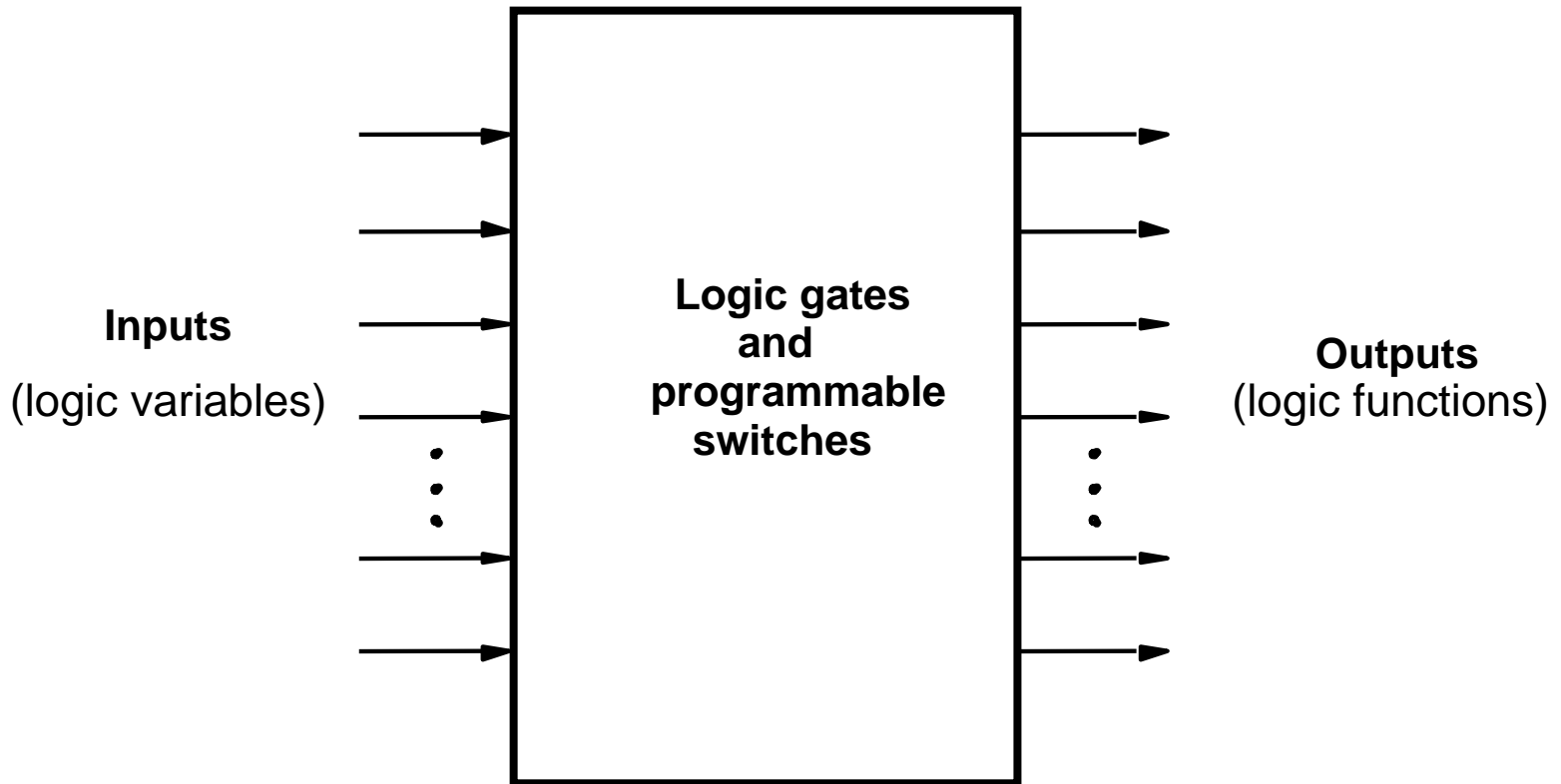


Figure 3.24. Programmable logic device as a black box.

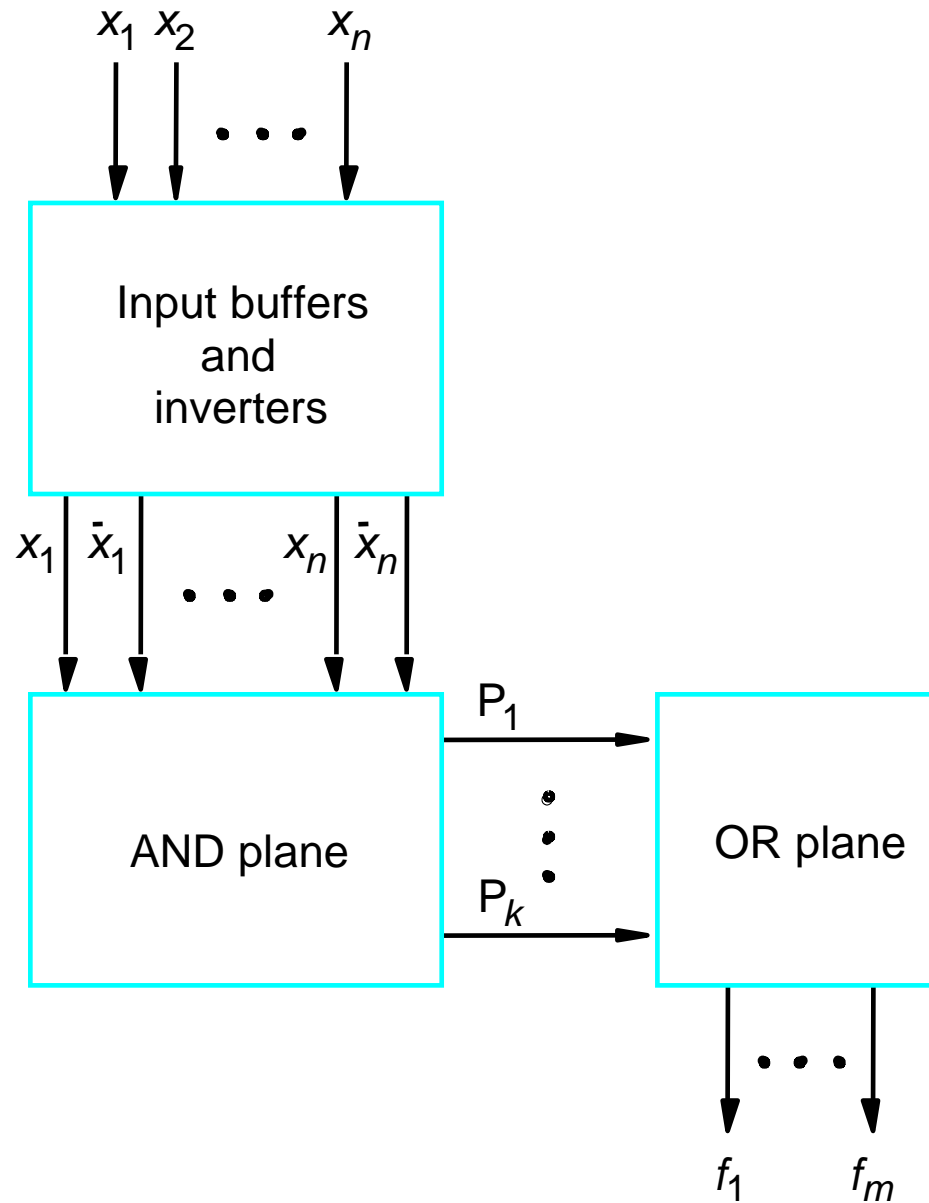


Figure 3.25. General structure of a PLA.

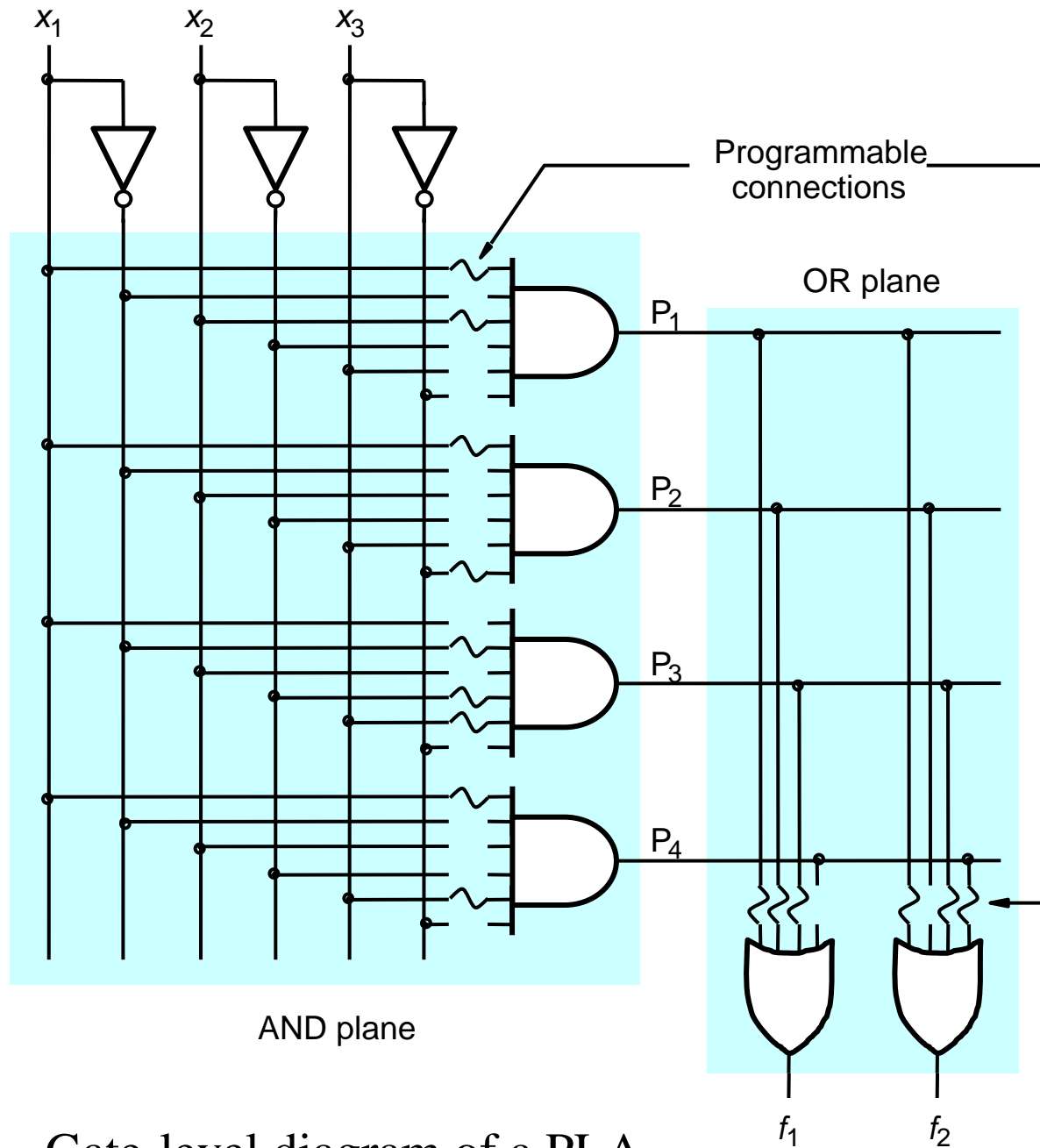


Figure 3.26. Gate-level diagram of a PLA.

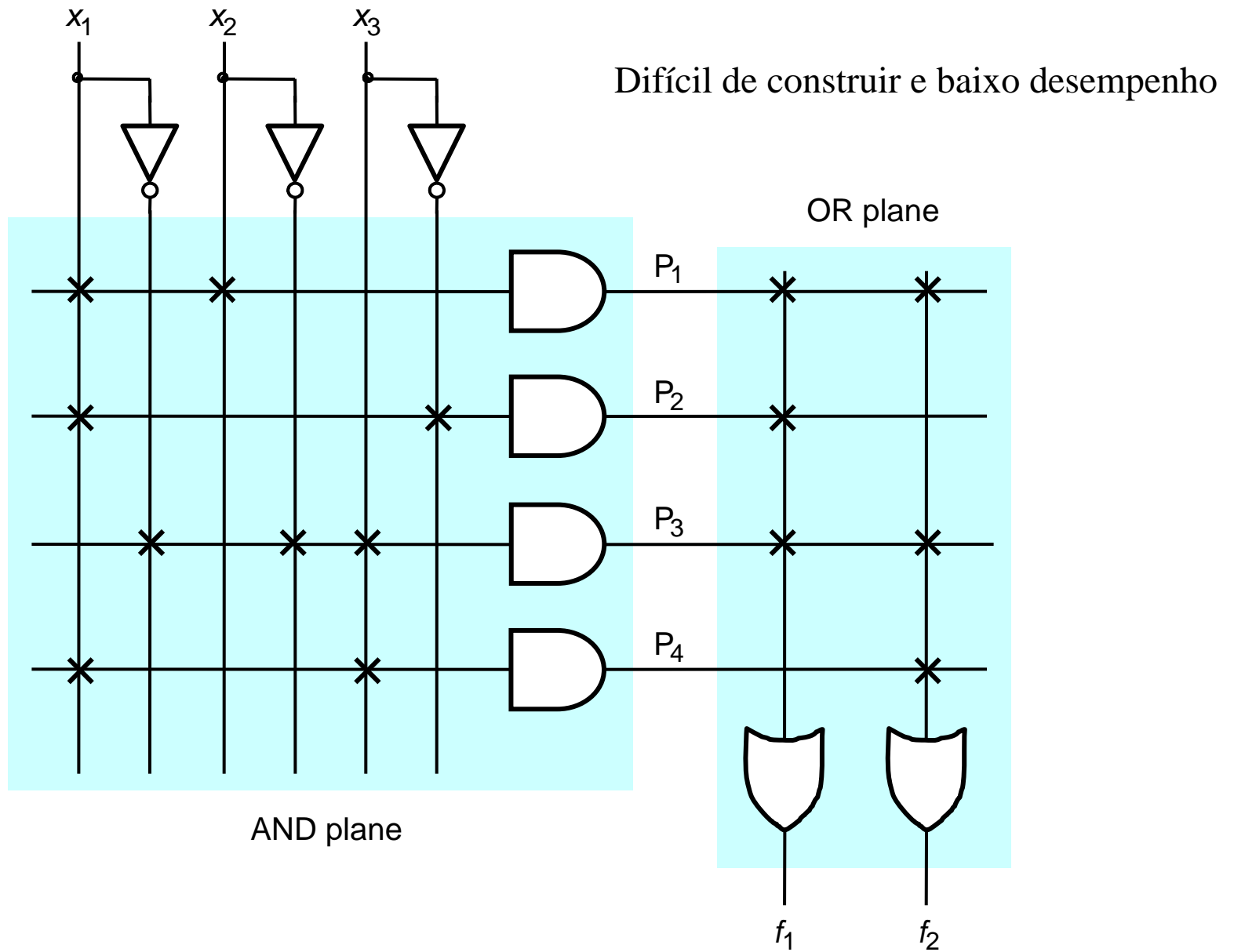


Figure 3.27. Customary schematic for the PLA in Figure 3.26.

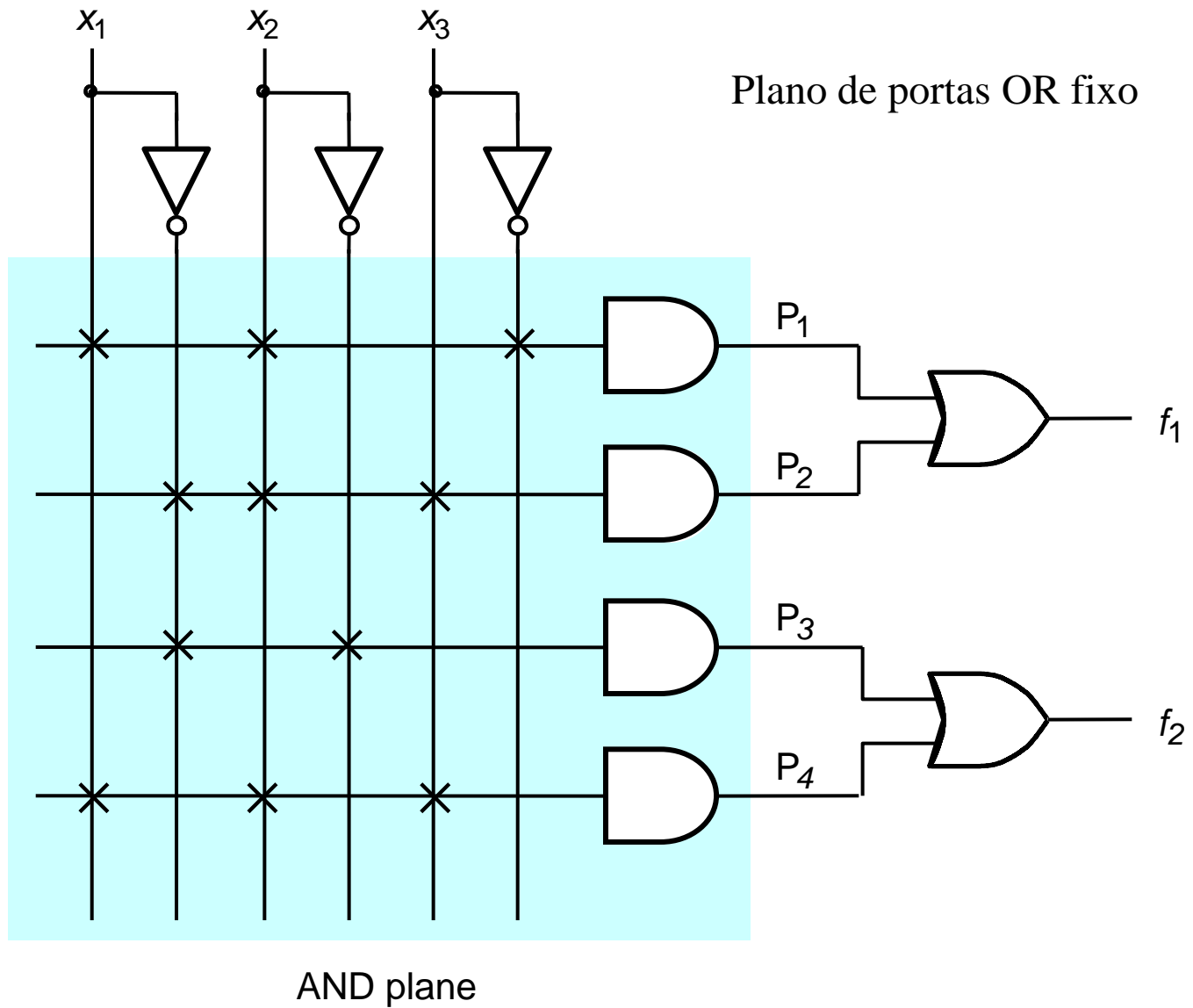


Figure 3.28. An example of a PAL

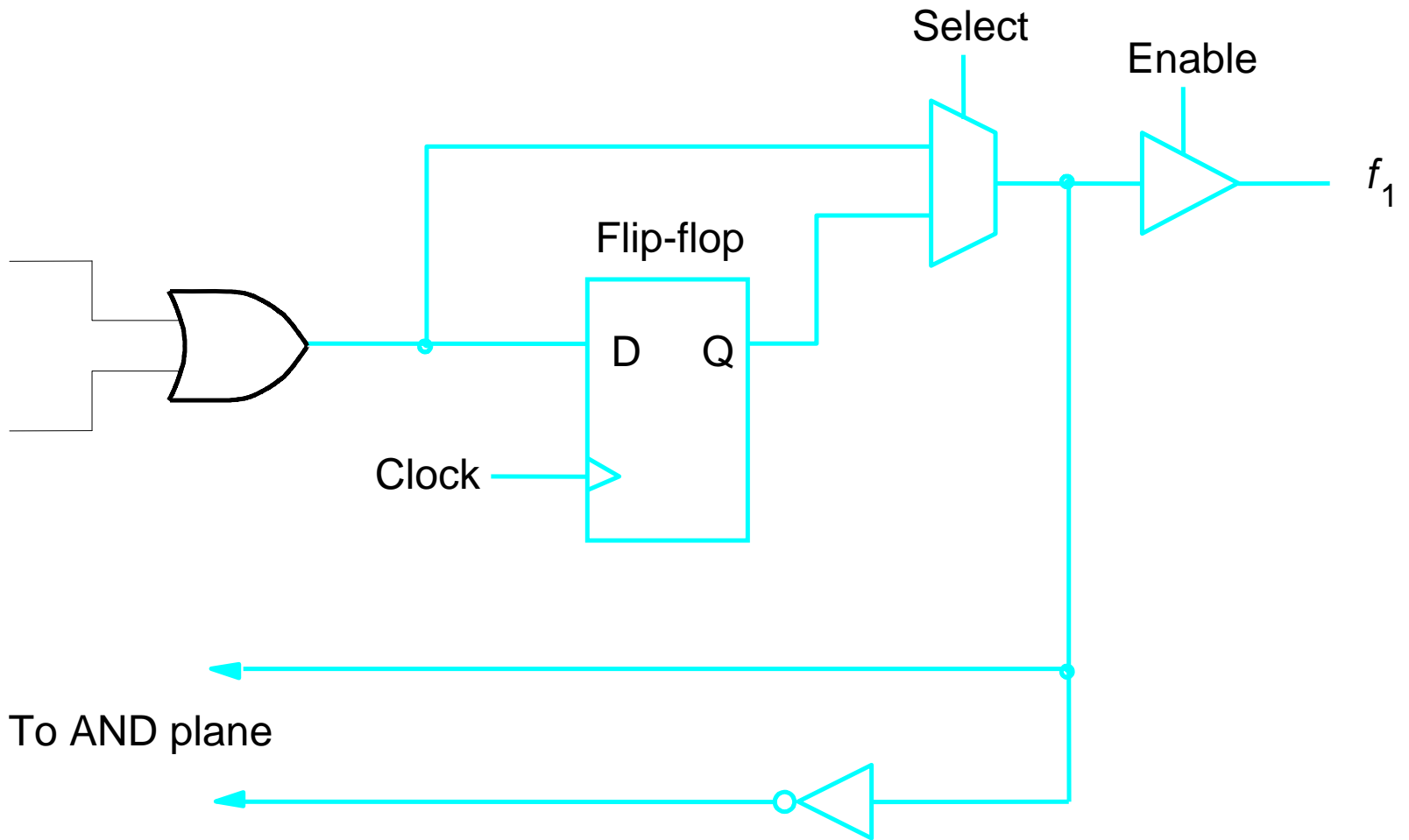


Figure 3.29. Extra circuitry added to OR-gate from Figure 3.28.



Figure 3.30. A PLD programming unit (courtesy of Data IO Corp).

 


Figure 3.31. A PLCC package with socket.

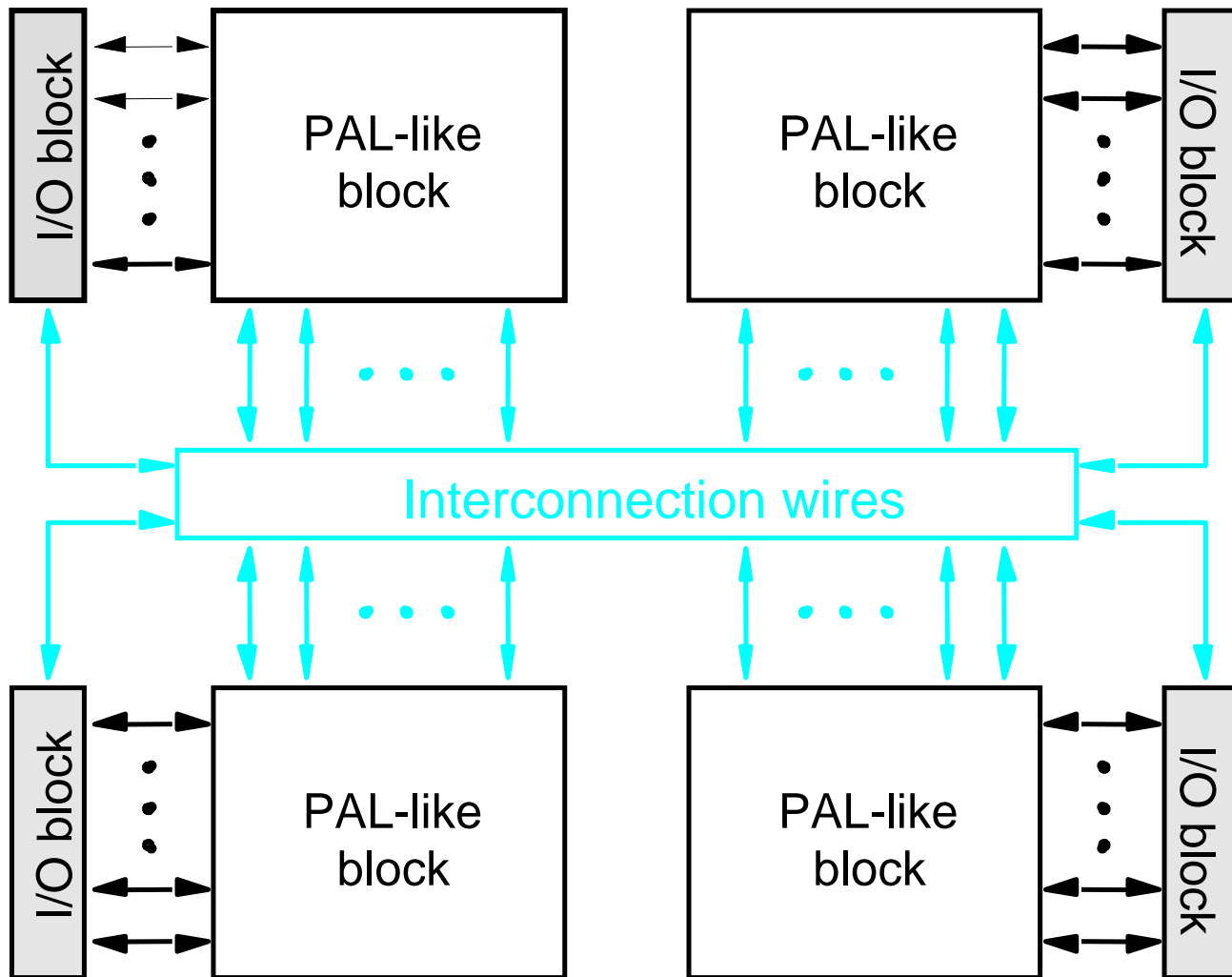


Figure 3.32. Structure of a complex programmable logic device (CPLD).



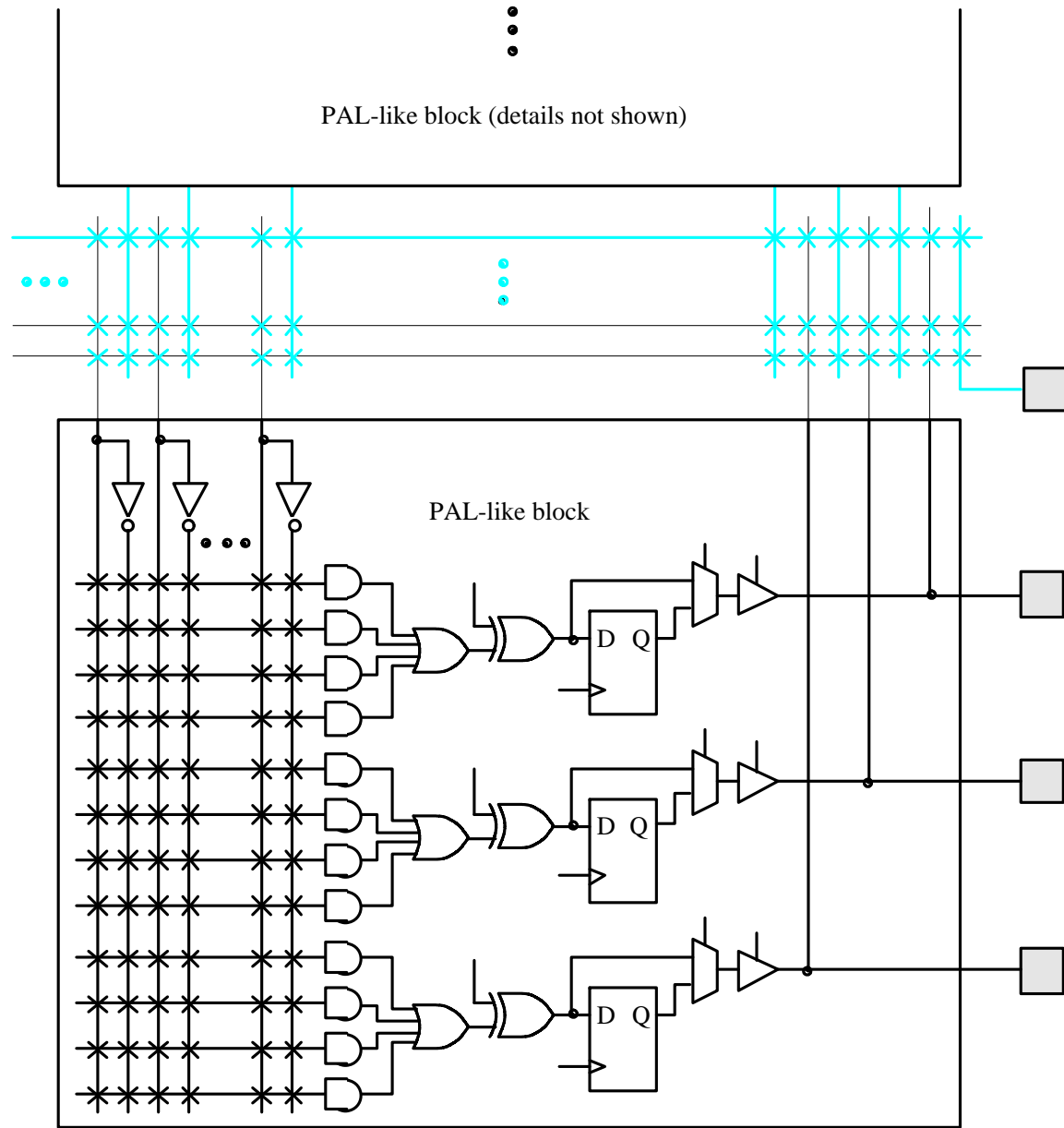


Figure 3.33. A section of the CPLD in Figure 3.32.

 


 (a) CPLD in a Quad Flat Pack (QFP) package




(b) JTAG programming

Figure 3.34. CPLD packaging and programming.

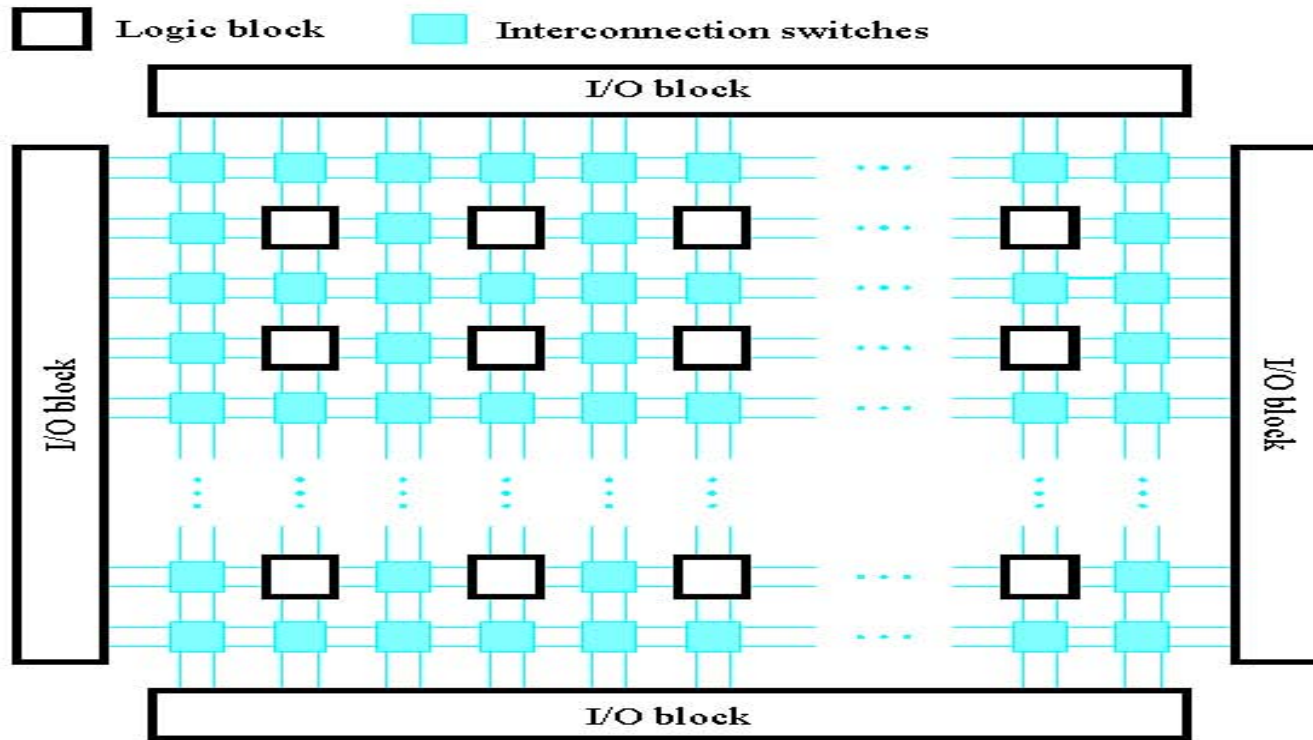


(a) General structure of an FPGA

 

(b) Pin grid array (PGA) package (bottom view)


Figure 3.35. A field-programmable gate array (FPGA).

 

(a) Circuit for a two-input LUT

| x_1 | x_2 | f_1 |
|-------|-------|-------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

(b) $f_1 = \bar{x}_1\bar{x}_2 + x_1x_2$

 

(c) Storage cell contents in the LUT

Figure 3.36. A two-input lookup table (LUT).

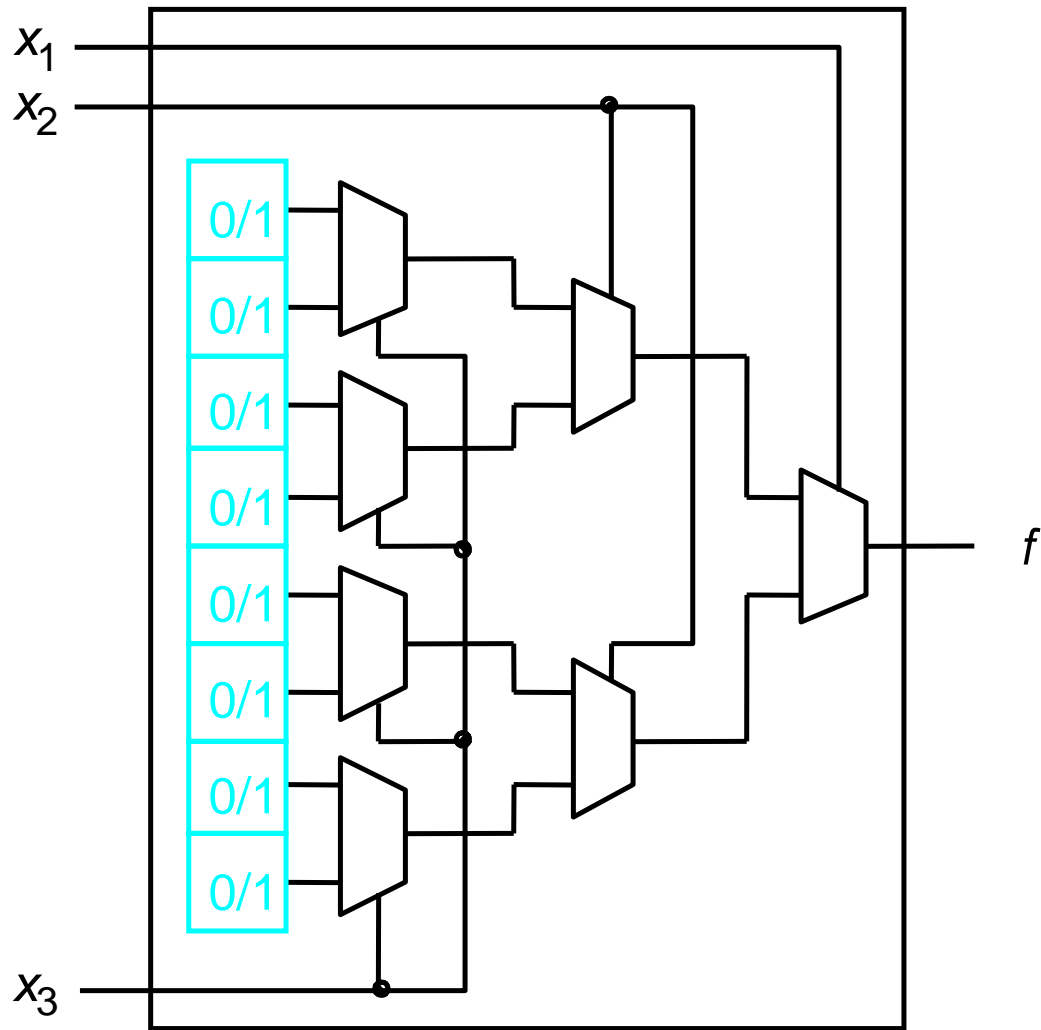


Figure 3.37. A three-input LUT.

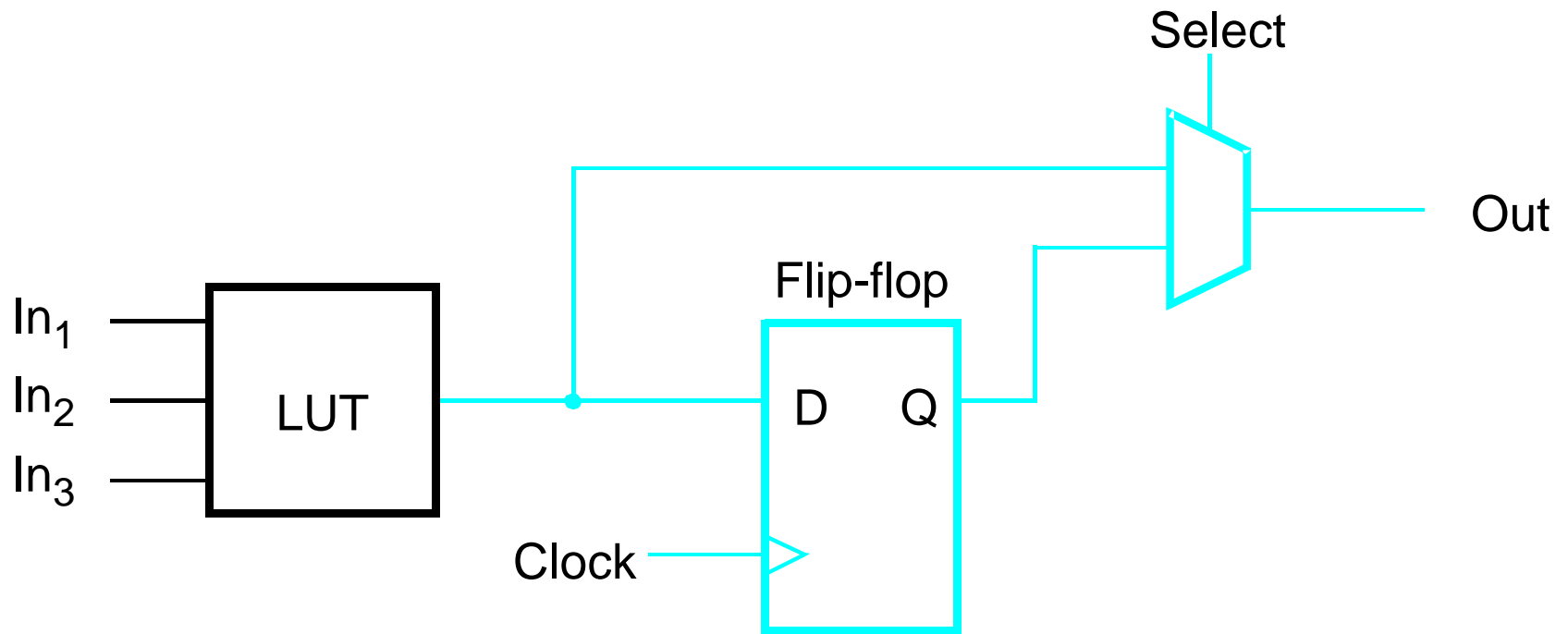


Figure 3.38. Inclusion of a flip-flop in an FPGA logic block.

 


Figure 3.39. A section of a programmed FPGA.

CIs construídos a partir de Células Padrões: ASIC (Aplicação Specific Integrated Circuit)

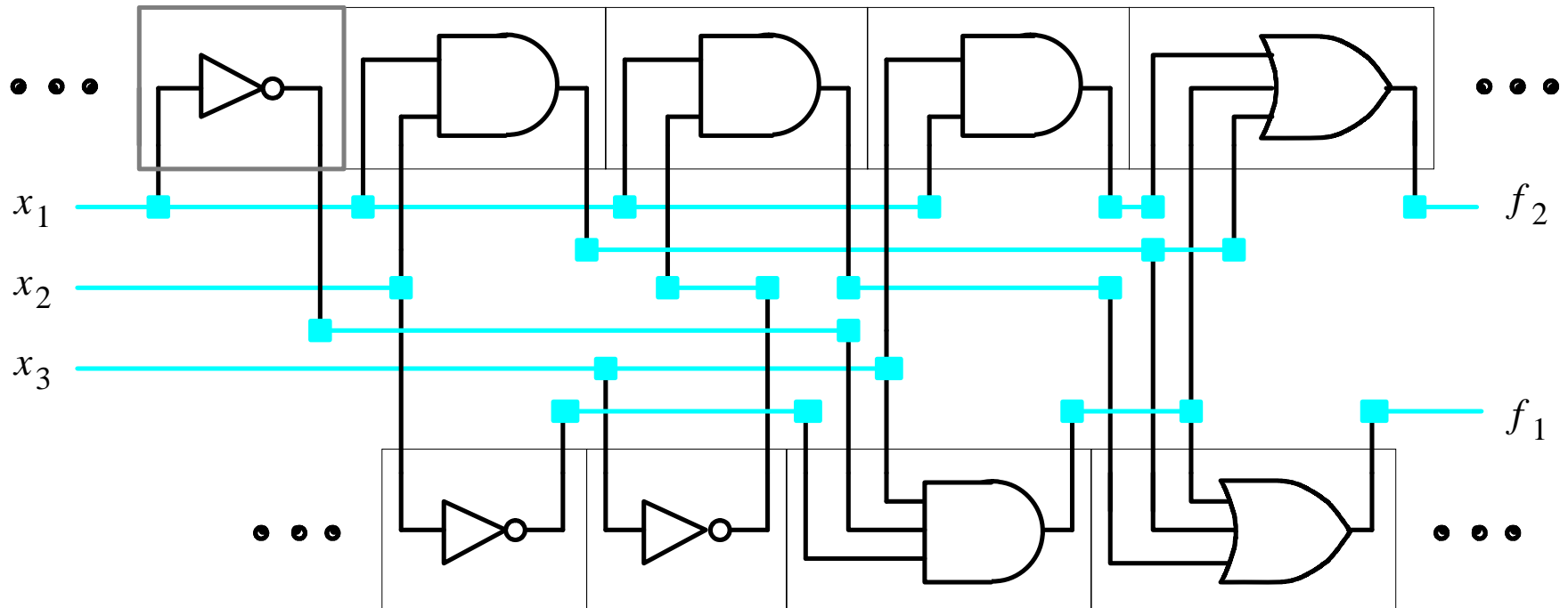


Figure 3.40. A section of two rows in a standard-cell chip

*Matriz de portas lógicas:
nesse caso todas as células/portas são idênticas*

 


Figure 3.41. A sea-of-gates gate array.


 



Figure 3.42. The logic function $f_1 = x_2\bar{x}_3 + x_1x_3$ in the gate array of Figure 3.41.

 Estrutura física de um transistor do tipo MMOS



(a) When $V_{GS} = 0\text{ V}$, the transistor is off

Figure 3.43a. NMOS transistor when turned off.

 

(b) When $V_{GS} = 5\text{ V}$, the transistor is on

Figure 3.43b. NMOS transistor when turned on.

Fábrica Virtual de Circuito Integrado

- http://www.necel.com/v_factory/en/index.html