

SCE 0110 -
Elementos de Lógica Digital I

**Flip-Flops, Registradores e
Contadores (continuação)**

Prof. Dr. Vanderlei Bonato


 



Figure 7.7. Gated SR latch with NAND gates.

 


(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

 

(d) Timing diagram

Figure 7.8. Gated D latch.



 



Figure 7.9. Setup and hold times.

 

(a) Circuit

 

(b) Timing diagram

 

(c) Graphical symbol

Figure 7.10. Master-slave D flip-flop.

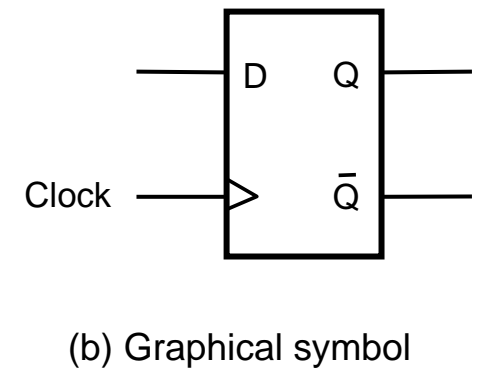
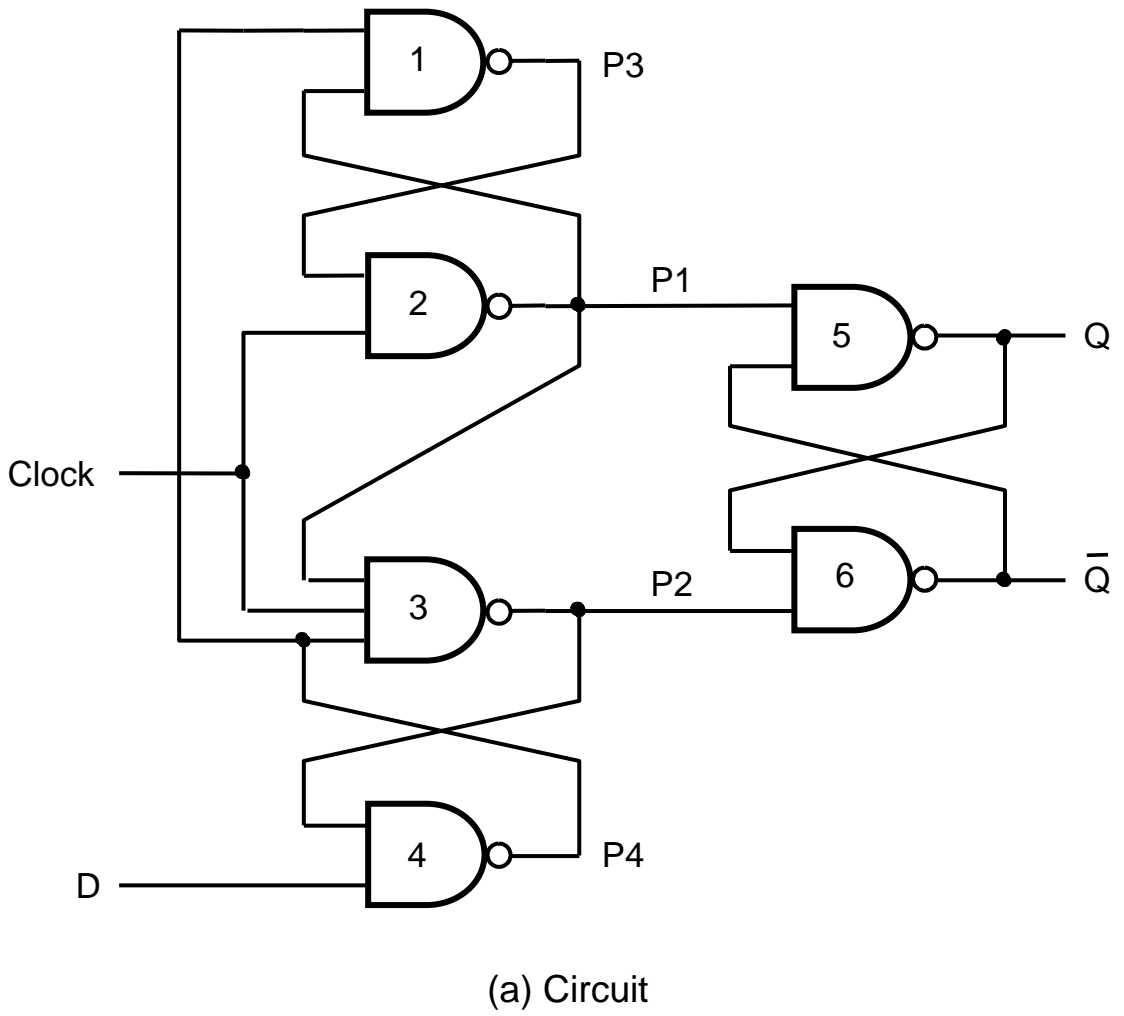


Figure 7.11. A positive-edge-triggered D flip-flop.



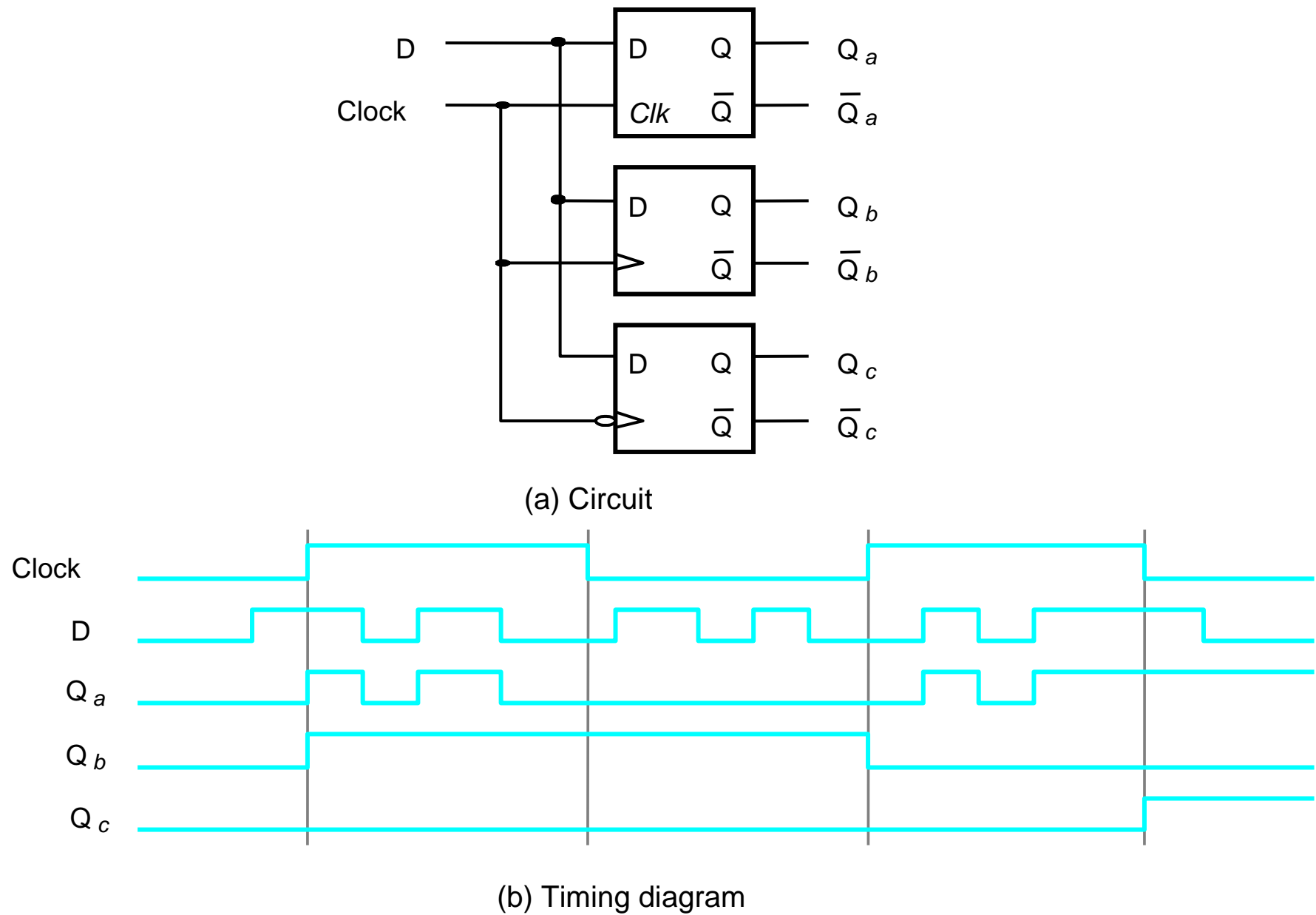


Figure 7.12. Comparison of level-sensitive and edge-triggered D storage elements.

 


(a) Circuit

 


(b) Graphical symbol

Figure 7.13. Master-slave D flip-flop with *Clear* and *Preset*.

 

(a) Circuit

 

(b) Graphical symbol

Figure 7.14. Positive-edge-triggered D flip-flop with *Clear* and *Preset*.


 



Figure 7.15. Synchronous reset for a D flip-flop.

 


(a) Circuit

T	$Q(t+1)$
0	$\underline{Q}(t)$
1	$\overline{Q}(t)$

(b) Truth table

 


(c) Graphical symbol

 

(d) Timing diagram


Figure 7.16. T flip-flop.

 

(a) Circuit


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

Figure 7.17. JK flip-flop.

 

(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

(b) A sample sequence

Figure 7.18. A simple shift register.

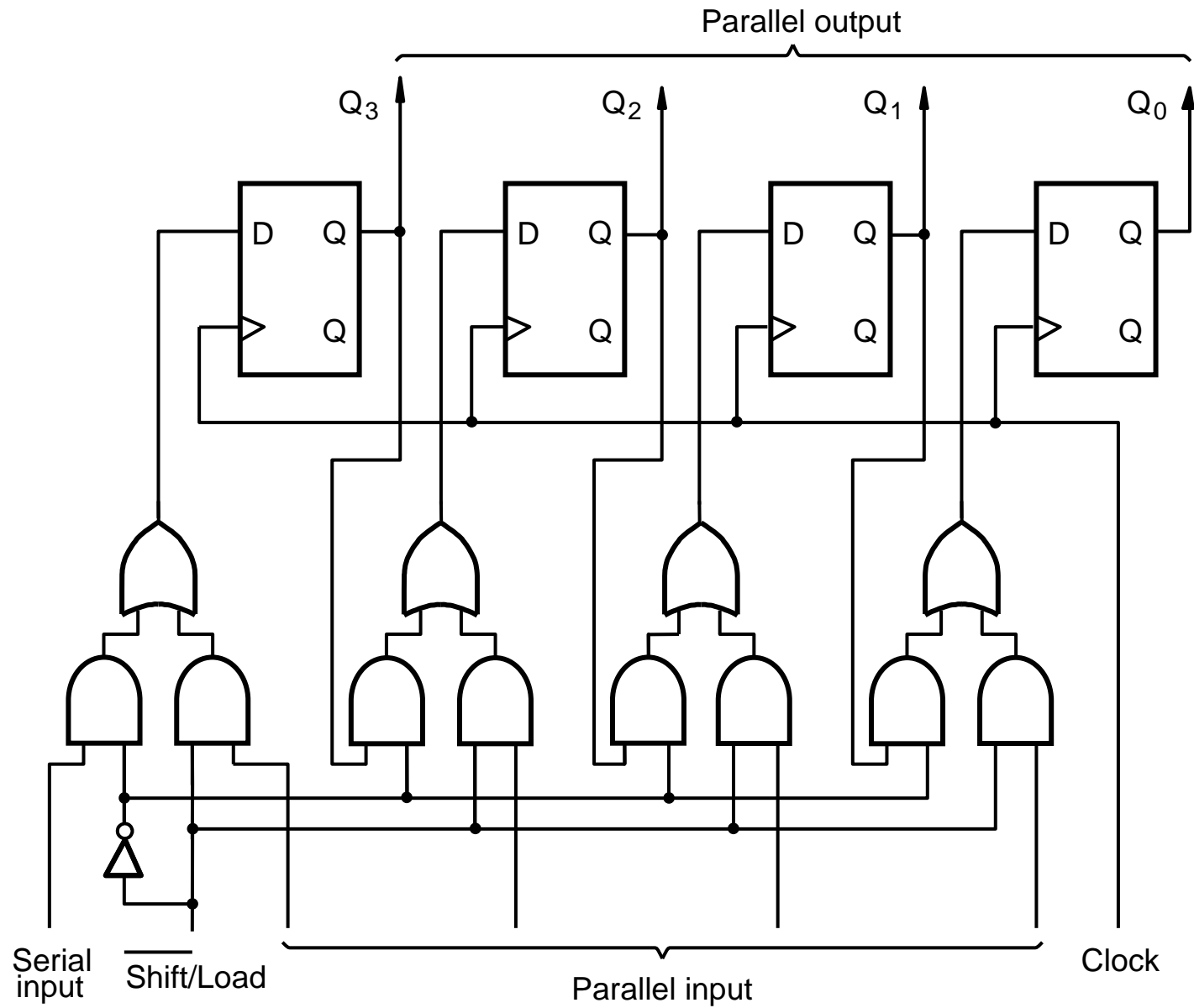


Figure 7.19. Parallel-access shift register.