

SCE 0117 -
Introdução à Lógica Digital

**Introdução aos circuitos lógicos
(continuação)**


Prof. Vanderlei Bonato

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$


Figure 2.17 Three-variable minterms and maxterms.

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Figure 2.18. A three-variable function.

 

 
(a) A minimal sum-of-products realization




(b) A minimal product-of-sums realization

Figure 2.19. Two realizations of a function in Figure 2.18.

- Estudar os exemplos 2.3 e 2.4

 


(a) NAND gates

 


(b) NOR gates

Figure 2.20. NAND and NOR gates.

 

 (a) $\overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$



(b) $\overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$

Figure 2.21. DeMorgan's theorem in terms of logic gates.

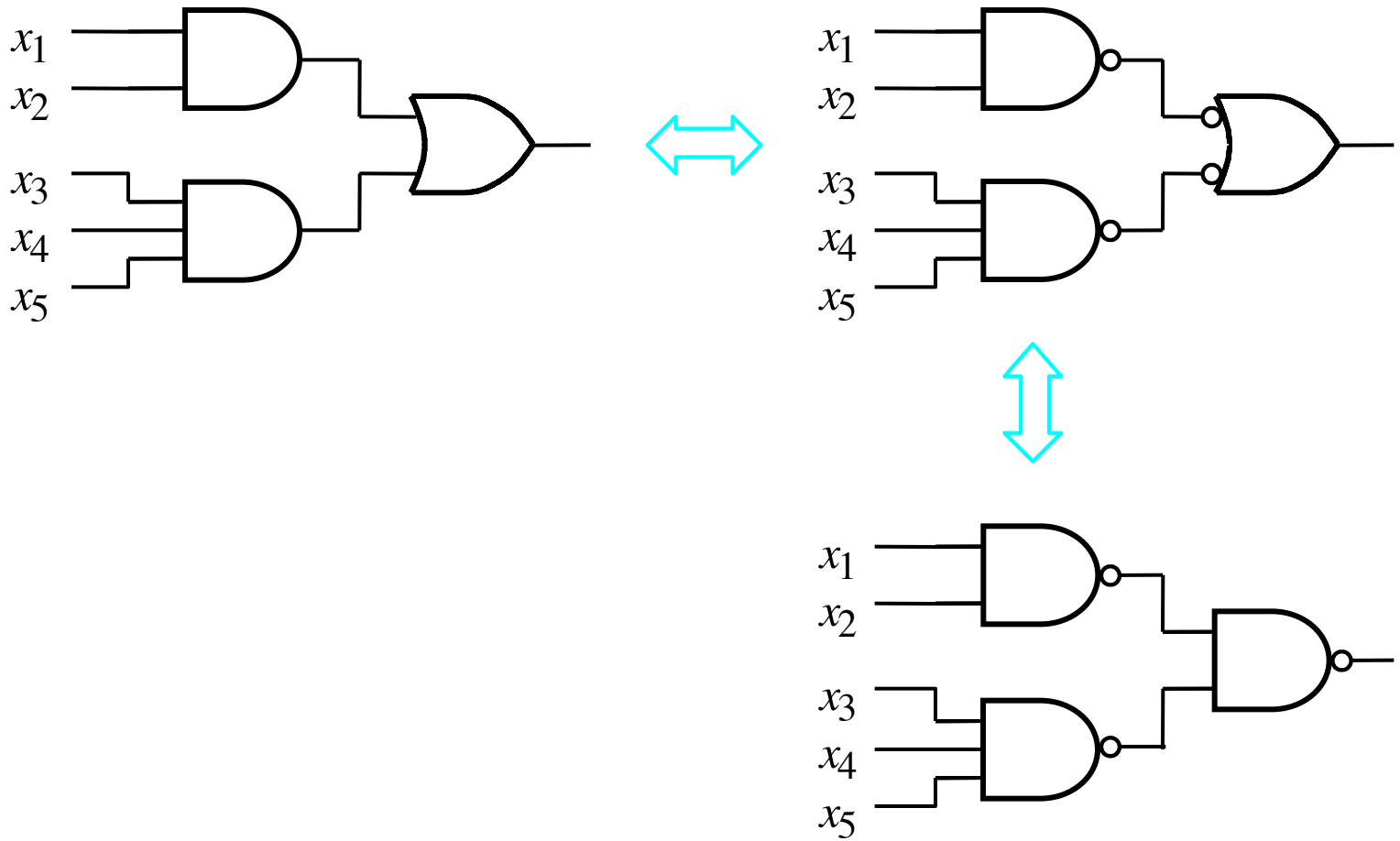


Figure 2.22. Using NAND gates to implement a sum-of-products.



 


Figure 2.23. Using NOR gates to implement a product-of sums.

- Estudar os exemplos 2.6 e 2.7

 


(a) POS implementation

 


(b) NOR implementation

Figure 2.24 NOR-gate realization of the function in Example 2.6.

 

(a) SOP implementation

 


(b) NAND implementation


Figure 2.25. NAND-gate realization of the function in Example 2.7.

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Figure 2.26. Truth table for a three-way light control.

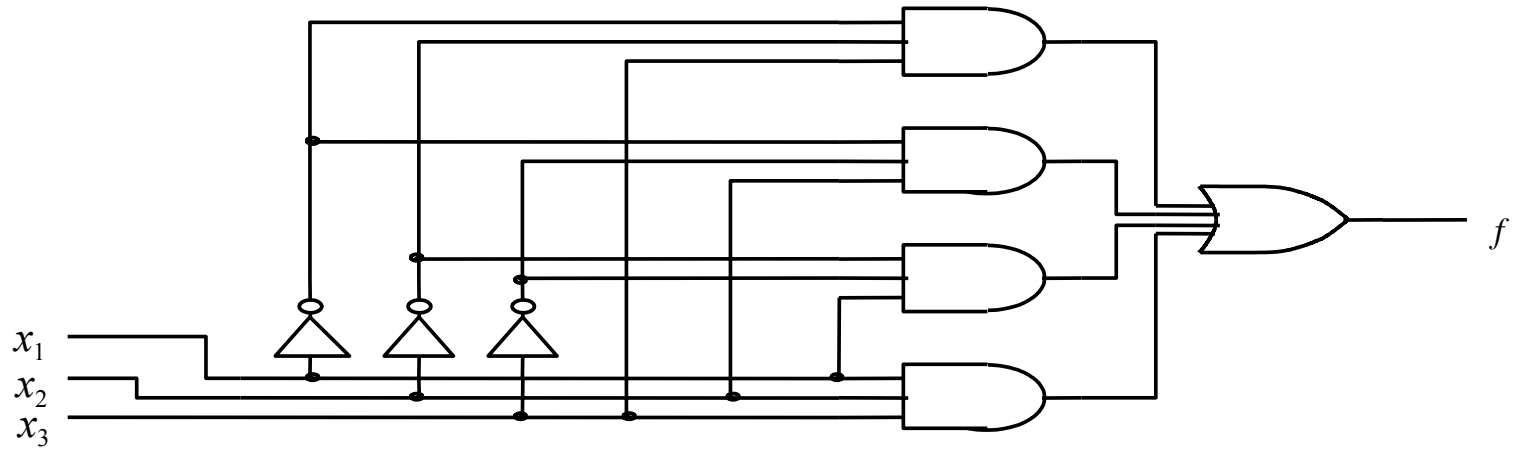

(a) Sum-of-products realization

 


(b) Product-of-sums realization


Figure 2.27. Implementation of the function in Figure 2.26.

s	x_1	x_2	$f(s, x_1, x_2)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

 

(c) Graphical symbol

s	$f(s, x_1, x_2)$
0	x_1
1	x_2

(d) More compact truth-table representation

Figure 2.28. Implementation of a multiplexer.

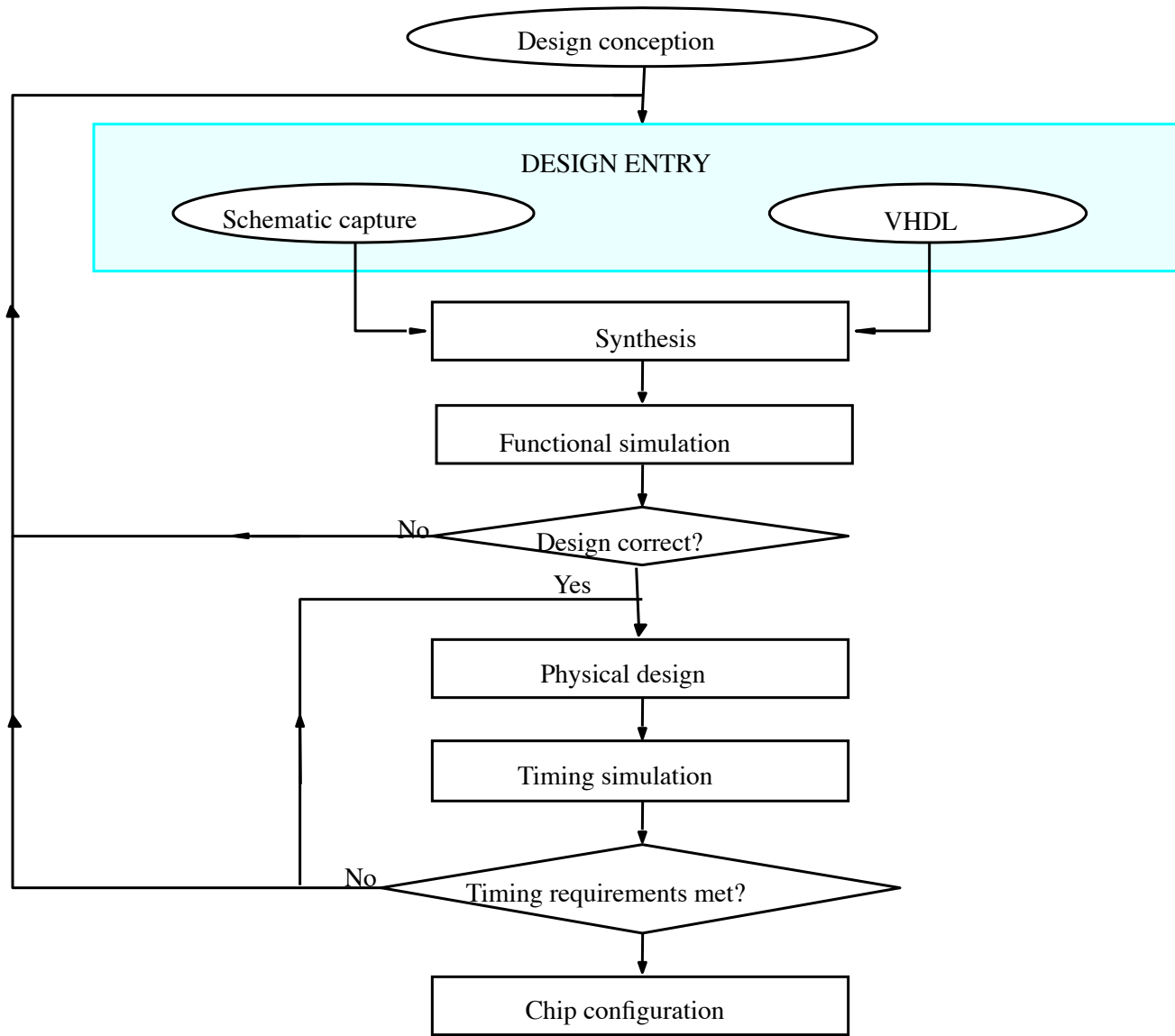


Figure 2.29. A typical CAD system.

 


Figure 2.30. A simple logic function.

```
ENTITY example1 IS
    PORT ( x1, x2, x3      : IN  BIT ;
          f                : OUT BIT ) ;
END example1 ;
```

Figure 2.31. VHDL entity declaration for the circuit in Figure 2.30.

```
ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3) ;
END LogicFunc ;
```

Figure 2.32. VHDL architecture for the entity in Figure 2.31.

```

ENTITY example1 IS
    PORT ( x1, x2, x3 : IN    BIT ;
          f           : OUT  BIT ) ;
END example1 ;

ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3) ;
END LogicFunc ;

```

Figure 2.33. Complete VHDL code for the circuit in Figure 2.30.

```

ENTITY example2 IS
    PORT ( x1, x2, x3, x4 : IN    BIT ;
          f, g           : OUT  BIT ) ;
END example2 ;

ARCHITECTURE LogicFunc OF example2 IS
BEGIN
    f <= (x1 AND x3) OR (NOT x3 AND x2) ;
    g <= (NOT x3 OR x1) AND (NOT x3 OR x4) ;
END LogicFunc ;

```

Figure 2.34. VHDL code for a four-input function.



 



Figure 2.35. Logic circuit for the code in Figure 2.34.

 


(a) Function A

 

(b) Function B

 


(c) Function C

 


(d) Function f

Figure 2.36. The Venn diagrams for Example 2.11.

 

(a)

 

(b)

Figure P2.1. Two attempts to draw a four-variable Venn diagram.

 


Figure P2.2. A four-variable Venn diagram.

 


Figure P2.3. A timing diagram representing a logic function.

 


Figure P2.4. A timing diagram representing a logic function.